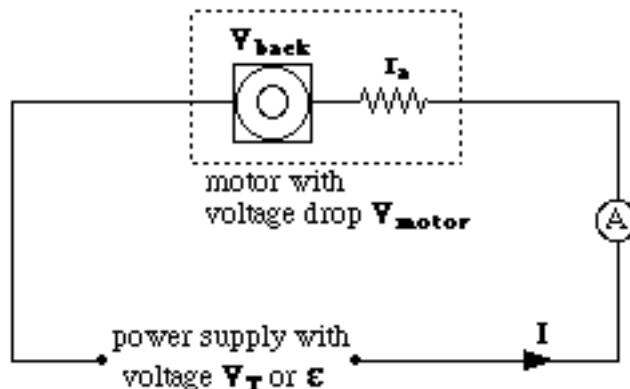


Back EMF in a Motor

An electric motor has the same design as a generator; the latter changes mechanical energy to electrical energy and the former, vice versa.

- A current in the armature of a motor turns in the magnetic field according to the **RHR**, with \mathbf{F}_{mag} creating the necessary torque.
- BUT the turning armature, by the nature of its motion in the field \mathbf{B} , has an EMF induced in it (just like a generator).
- As expected, this EMF opposes the voltage of the source that created it; that is, the motor becomes a generator as soon as it is turned on, and the opposing (or counter, or back) EMF will increase with increasing frequency.
- However, the applied EMF overcomes this "reverse emf" and makes the current flow in the direction suggested by the applied EMF; in effect, the reverse EMF acts as a *brake* on incoming current and limits it.

Now examine the following schematic diagram:



The only load in this circuit is a motor with a voltage drop V_{motor} . Meanwhile, if the motor is plugged into an electrical outlet, then the voltage supplied is the **EMF** provided by BC Hydro. By inspection of the diagram, we see that the voltage supplied by the power supply must equal the voltage drop in the motor, or

$$V_{\text{motor}} = \epsilon$$

Note that this voltage drop in the motor V_{motor} is caused by *two* factors:

- the relatively small resistance in the armature r_a , which produces a voltage drop equal to $V_a = I r_a$
- the *back* EMF produced by the rotating armature (V_{back}) which also acts like a voltage drop.

Therefore, the total voltage drop across the motor V_{motor} is $V_{\text{motor}} = V_{\text{back}} + I r_a$

→ which can also be written as $\epsilon = V_{\text{back}} + I r_a$ (remember, $\epsilon = V_{\text{motor}}$)

Note that this equation tells us that the power supplied by BC Hydro will *always* deliver more voltage than the back EMF produced by the motor. It can also be re-arranged to read

$$V_{\text{back}} = \epsilon - I r_a$$

→ which is what you see on the formula sheet.

Example #9: A motor operating at full speed draws a current of 4.0 A when connected to a 110 V source. If the motor has an armature resistance of 3.5 Ω , what is the back EMF at full speed?

(see Induction Ex 9 for answer)

In this example, emphasis was placed on the motor operating at full speed. In fact, the back EMF varies *directly* with the frequency of rotation, so that if the armature is rotating at less than full speed, V_{back} decreases. This causes less overall resistance in the circuit, so that the current will *increase*. Even worse, if the motor's armature is jammed so that it can't turn at all, then:

$$V_{\text{back}} = 0 \quad \text{and} \quad \epsilon = I r_a$$

This is not a good thing:

- if the resistance in the armature is small, then the current running through it will be high;
- the power lost to heat ($P = I^2 r_a$) will be much larger; in fact, the motor will likely overheat as a result.

Example #10: A 120 V dc motor has an armature resistance of 5.0 Ω and draws 6.0 A when it is operating normally.

- a) What is the starting current of the motor just before the armature begins to turn
- b) What is the back EMF when it is operating properly?

(see Induction Ex 10 for answer)

Finally, you must remember that if the power source is a battery, the *terminal voltage* V_T must be used in place of \mathcal{E} in the motor equation.

Example #11: A power supply of EMF 6.0 V and internal resistance $0.50\ \Omega$ is used to run a motor. When the motor is jammed, the current is 3.0 A, but when it is allowed to run freely, current is 1.8 A.

- a) What is the resistance of the armature of the motor?
- b) What is the back EMF of the motor when running freely?

(see Induction Ex 11 for answer)

In terms of overall power used in a motor:

Power supplied = heat in armature + mechanical power output

➤ or, $IV_T = I^2r_a + IV_{\text{back}}$

The efficiency of a motor can be determined based on its output power compared to power supplied.

Example #12: Determine the efficiency of a motor which has a back EMF of 8.0 V when a source voltage of 12.0 V is supplied.

(see Induction Ex 12 for answer)